

# BOOLEAN\_FUNCTION\_MINIMIZATION

## AIM:

To implement the given logic function verify its operation in Quartus using Verilog programming.

$$F1 = A'B'C'D' + AC'D' + B'CD' + A'BCD + BC'D$$

$$F2 = xy'z + x'y'z + w'xy + wx'y + wxy$$

## Equipment Required:

Hardware – PCs, Cyclone II , USB flasher

Software – Quartus prime

## Theory


## Logic Diagram

## Procedure

1. Type the program in Quartus software.
2. Compile and run the program.
3. Generate the RTL schematic and save the logic diagram.
4. Create nodes for inputs and outputs to generate the timing diagram.
5. For different input combinations generate the timing diagram.
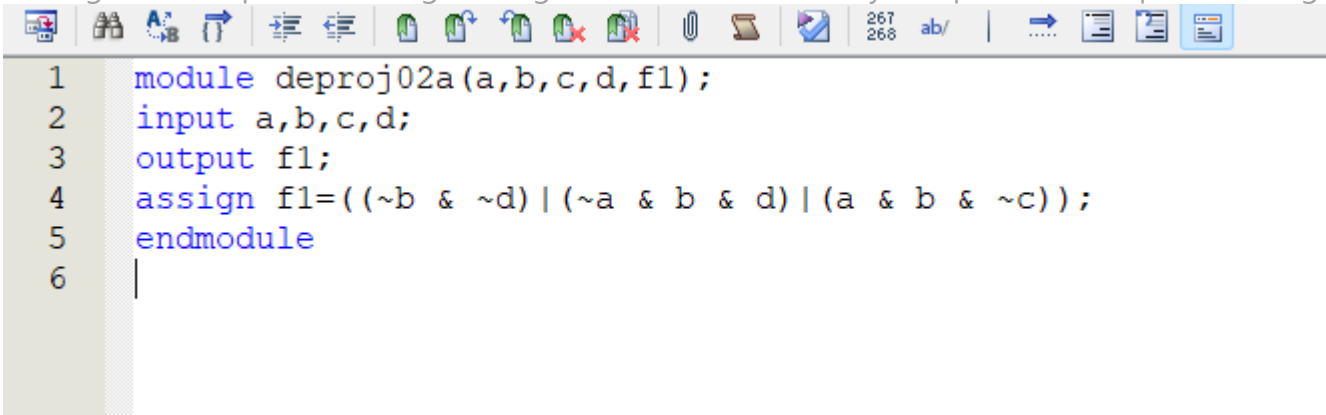
## Program:

/\* Program to implement the given logic function and to verify its operations in quartus using Verilog programming.



```
1 module deproj02a(a,b,c,d,f1);
2 input a,b,c,d;
3 output f1;
4 assign f1=((~b & ~d) | (~a & b & d) | (a & b & ~c));
5 endmodule
6 |
```

Quartus II 64-Bit - C:/altera/13.0sp2/boolean - boolean

File Edit View Project Assignments Processing Tools Window Help



boolean

db/boolean.v


Compilation Report - boolean


```
1 module boolean(w,x,y,z,f2);
2 input w,x,y,z;
3 output f2;
4 assign f2=((~y&z)|(x&y)|(w&y));
5 endmodule
6
```

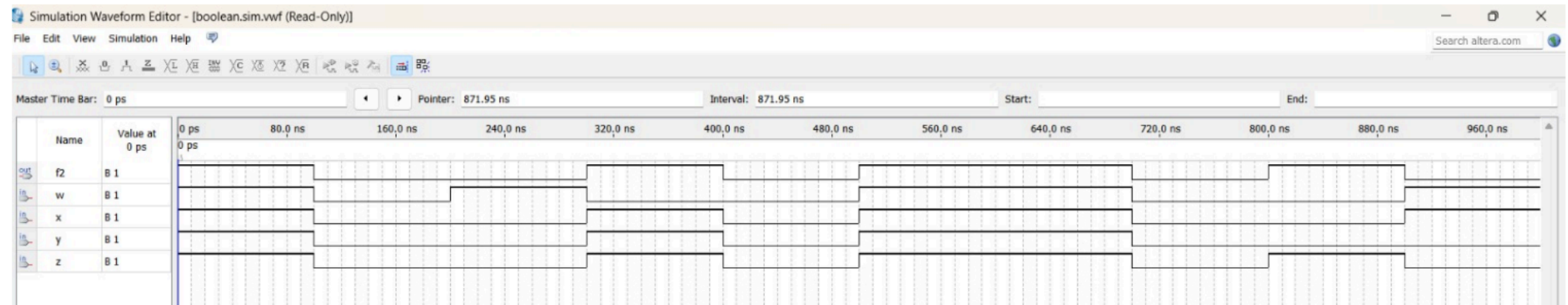 Developed by: Akash M  
Register Number: 24900103  
RTL realization output



RTL

 

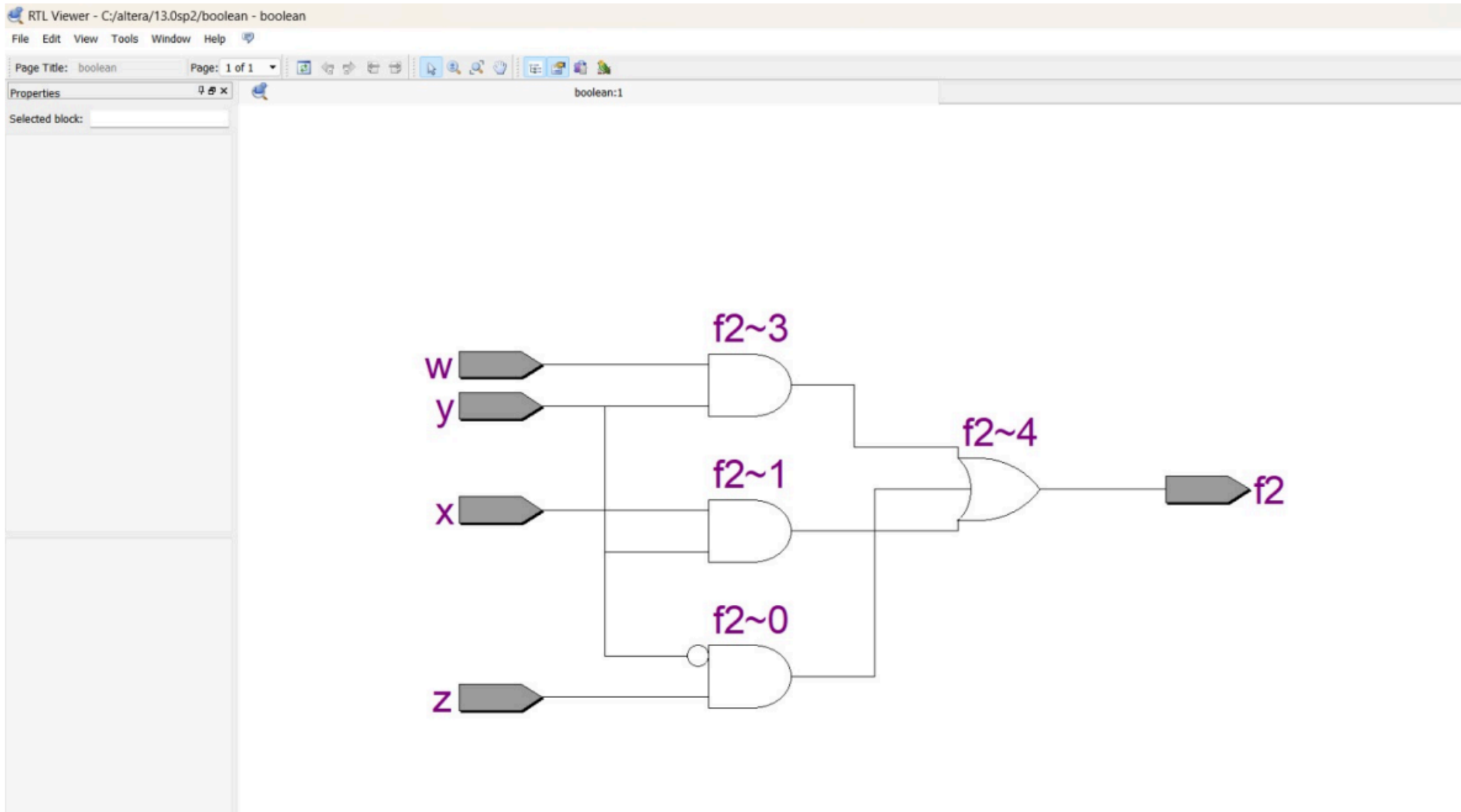

Truth Table

A	B	C	D	A'B'C'D'	AC'D'	B'CD'	A'BCD	BC'D	F1
0	0	0	0	1	0	0	0	0	1
0	0	0	1	0	0	0	0	0	0
0	0	1	0	0	0	0	0	0	0
0	0	1	1	0	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0
0	1	0	0	0	0	0	0	1	1
0	1	1	0	0	0	0	0	0	0
0	1	1	1	0	0	0	1	0	1
1	0	0	0	0	1	0	0	0	1
1	0	0	1	0	0	0	0	0	0
1	0	1	0	0	0	1	0	0	1
1	0	1	1	0	0	0	0	0	0
1	1	0	0	0	1	0	0	0	1
1	1	0	1	0	0	0	0	1	1
1	1	1	0	0	0	0	0	0	0
1	1	1	1	0	0	0	0	0	0

W	X	Y	Z	$XY'Z$	$X'Y'Z$	$W'XY$	$WX'Y$	$WXY$	F2
0	0	0	0	0	0	0	0	0	0
0	0	0	1	1	0	0	0	0	1
0	0	1	0	0	0	0	0	0	0
0	0	1	1	1	0	0	0	0	0
0	1	0	0	0	0	0	0	0	0
0	1	0	1	1	1	0	0	0	1
0	1	1	0	0	0	0	1	0	1
0	1	1	1	1	0	0	1	0	1
1	0	0	0	0	0	0	0	0	0
1	0	0	1	1	0	0	0	0	0
1	0	1	0	0	0	0	0	1	0
1	0	1	1	1	0	0	0	1	0
1	1	0	0	0	0	1	0	0	0
1	1	0	1	1	1	0	0	0	0
1	1	1	0	0	0	0	0	1	1
1	1	1	1	1	0	0	0	1	1

**Result:** The implement of the given logic function and to verify its operation in Quartus using Verilog programming . Thus the given logic functions are implemented using and their operations are verified using Verilog programm